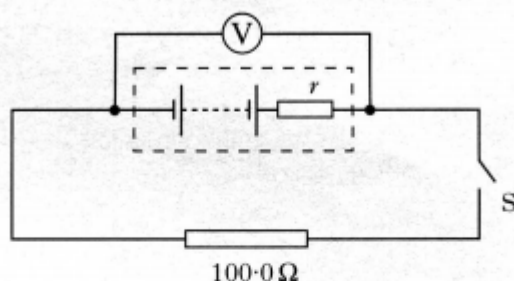


Exercise 12 - Emf and Internal Resistance

Past Paper Homework Questions

1. A pupil sets up the following circuit to measure the internal resistance r of a battery.




The reading on the voltmeter is 12.0 V when switch S is open. The reading drops to 10.0 V when switch S is closed.

The internal resistance of the battery is

- A 0.00 Ω
- B 0.05 Ω
- C 16.7 Ω
- D 20.0 Ω
- E 100.0 Ω

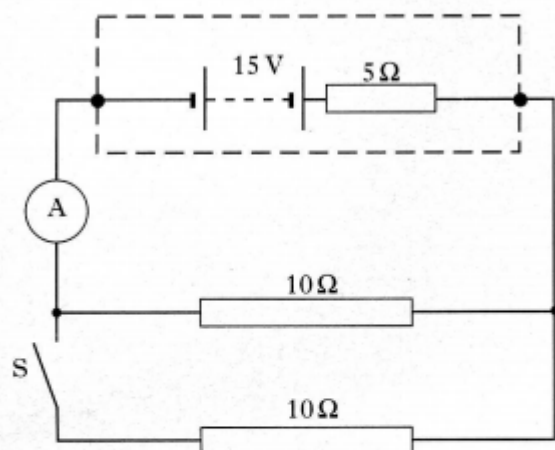
2. A battery, of e.m.f. 15 V and internal resistance 5 Ω , is connected to two 10 Ω resistors as shown. Switch S is initially open.



When switch S is closed, the reading on the ammeter changes

- A from 1 A to 2 A
- B from 1.5 A to 3 A
- C from 1 A to 1.5 A
- D from 1.5 A to 0.75 A
- E from 1 A to 0.6 A.

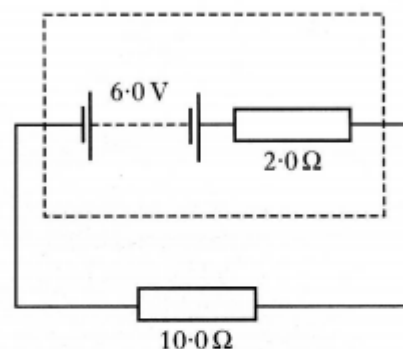
3. A battery has an e.m.f. of 6.0 V and an internal resistance of 2.0 Ω . It is connected to a 10.0 Ω resistor, as shown below.



The p.d. across the 10.0 Ω resistor is

- A 1.0 V
- B 1.2 V
- C 4.8 V
- D 5.0 V
- E 6.0 V.

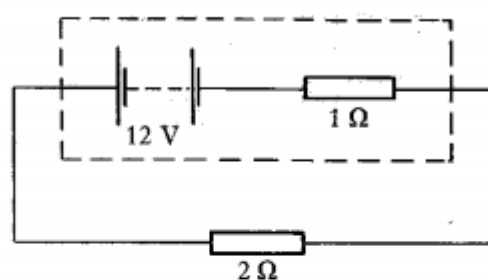
4. A battery of e.m.f. 12 V and internal resistance 1 Ω is connected across a 2 Ω resistor, as shown in the circuit below.



Which row in the following table shows the correct values for current, terminal potential difference and lost volts in this circuit?


	Current/A	t.p.d./V	lost volts/V
A	4	4	8
B	4	8	4
C	6	4	8
D	6	8	4
E	12	8	4

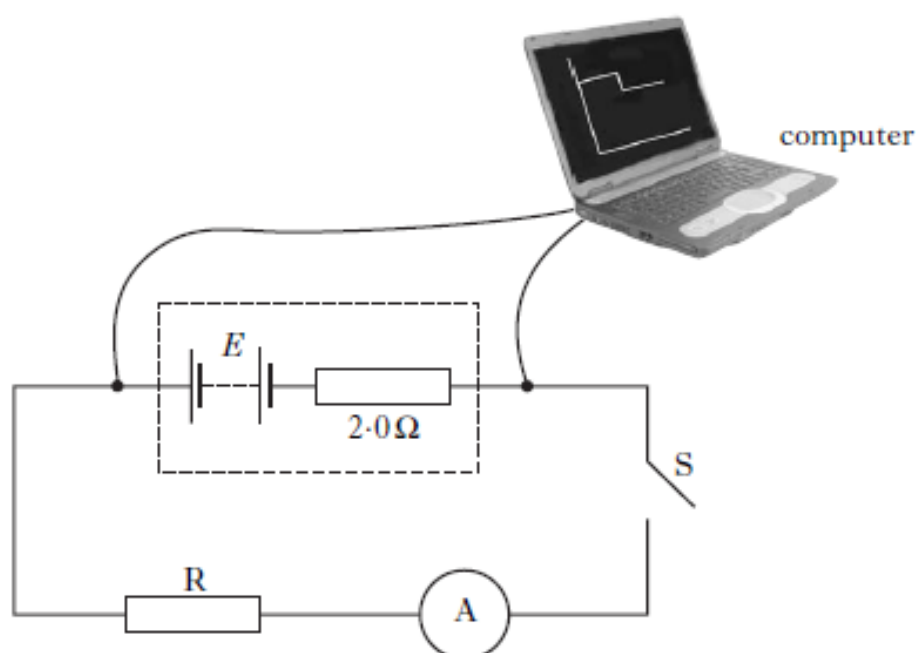5. A power supply of e.m.f. E and internal resistance $2.0\ \Omega$ is connected as shown.



The computer connected to the apparatus displays a graph of potential difference against time.

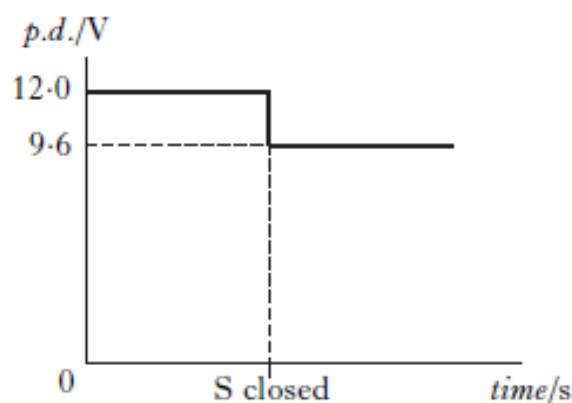
The graph shows the potential difference across the terminals of the power supply for a short time before and after switch S is closed.




- (a) State the e.m.f. of the power supply. 1
- (b) Calculate: 3
- (i) the reading on the ammeter after switch S is closed; 1
- (ii) the resistance of resistor R . 1

5. (cont.)

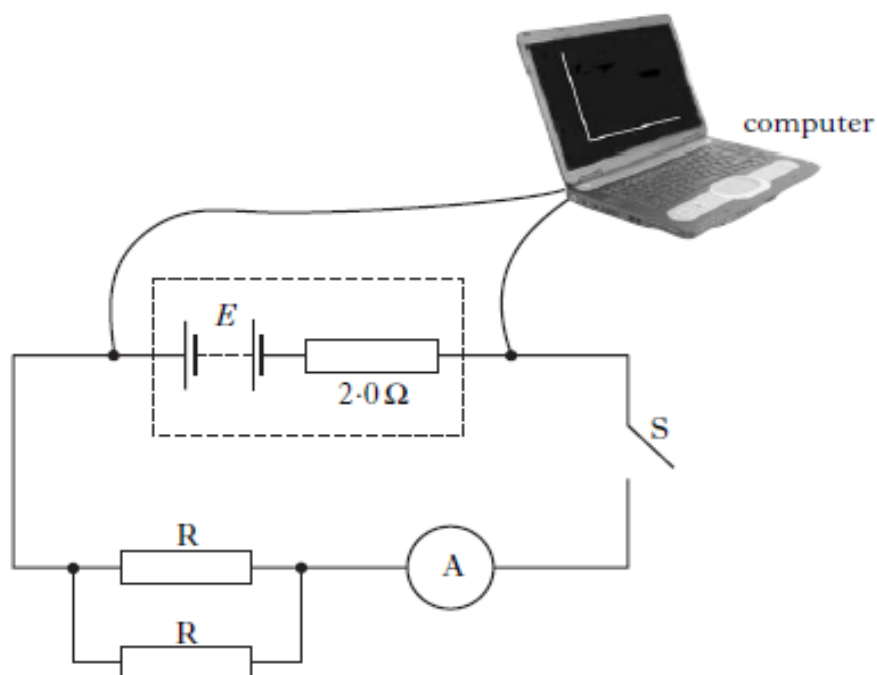- (c) Switch S is opened. A second identical resistor is now connected in parallel with R as shown.



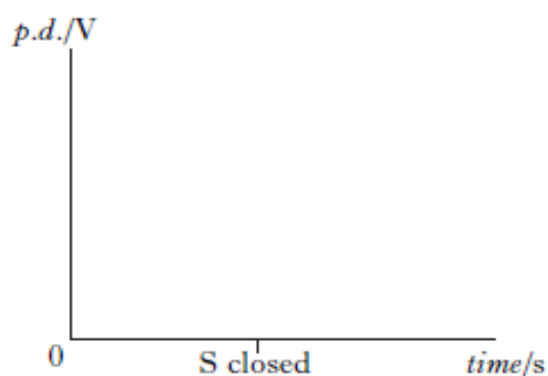The computer is again connected in order to display a graph of potential difference against time.



Copy and complete the new graph of potential difference against time showing the values of potential difference before and after switch S is closed.

3


(8)

6. Electrically heated gloves are used by skiers and climbers to provide extra warmth.



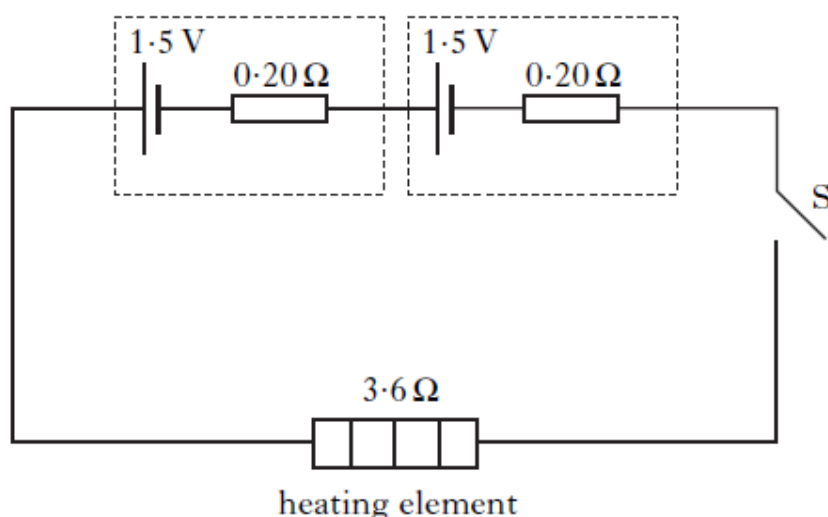- (a) Each glove has a heating element of resistance $3.6\ \Omega$.

Two cells, each of e.m.f. 1.5 V and internal resistance $0.20\ \Omega$, are used to operate the heating element.




Switch S is closed.


- | | |
|--|---|
| (i) Determine the value of the total circuit resistance. | 1 |
| (ii) Calculate the current in the heating element. | 3 |
| (iii) Calculate the power output of the heating element. | 3 |
- (b) When in use, the internal resistance of each cell gradually increases.
- What effect, if any, does this have on the power output of the heating element?
- Justify your answer.

4
(11)

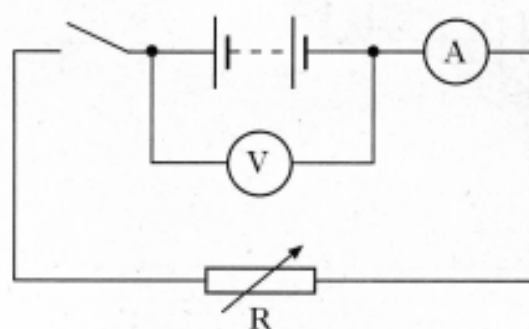7. (a) The following circuit is used to measure the e.m.f. and the internal resistance of a battery.



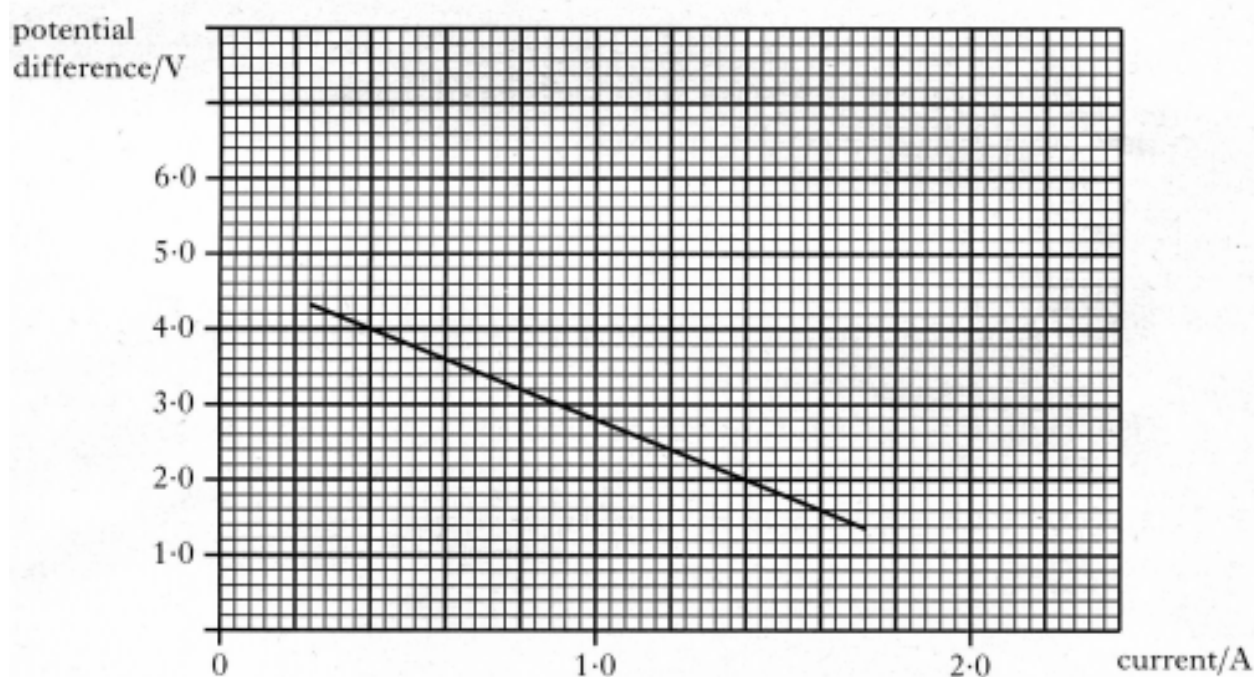
Readings of current and potential difference from this circuit are used to produce the following graph.



Use information from the graph to find:


- | | |
|--|---|
| (i) the e.m.f. of the battery, in volts; | 1 |
| (ii) the internal resistance of the battery. | 3 |
- (b) A car battery has an e.m.f. of 12 V and an internal resistance of 0.050Ω .
- | | |
|---|---|
| (i) Calculate the short circuit current for this battery. | 3 |
| (ii) The battery is now connected in series with a lamp. The resistance of the lamp is 2.5Ω . Calculate the power dissipated in the lamp. | 4 |

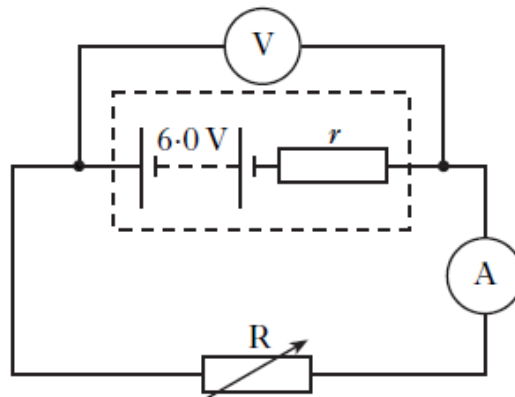8. A battery of e.m.f. 6.0 V and internal resistance, r , is connected to a variable resistor R as shown.



The graph shows how the current in the circuit changes as the resistance of R increases.

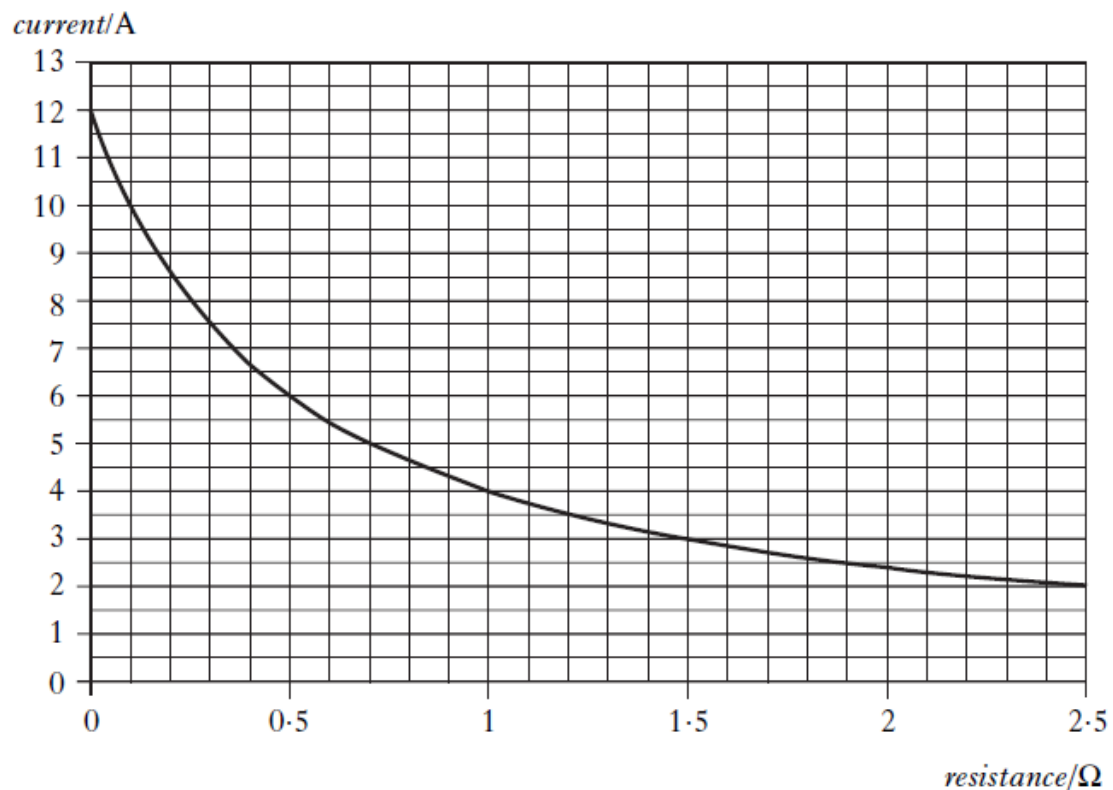The graph shows how the current in the circuit changes as the resistance of R increases.



- (a) Use information from the graph to calculate:

the lost volts in the circuit when the resistance of R is $1.5\ \Omega$;

4

- (b) The resistance of R is now increased.

What effect, if any, does this have on the lost volts?

You must justify your answer

2